



---

# ASSIGNMENT 4 - REPORT

---

Power Electronics and Applications



ELEC3204  
BY 470416309  
Vishant Prasad

## Contents

Section 1 - Steady – State Analysis and Concept Design .....	2
Section 2 - Simulation .....	4
Bibliography .....	10

# Assignment 4 – Report

## Forward Converter

Table 1: Forward Converter Specifications

Symbol	Description	Value
$P_{norm}$	Nominal Power Rating	240W
$V_{in}$	Nominal Input Voltage	330V
$V_o$	Nominal Output Voltage	12V
$f_{sw}$	Switching Frequency	100kHz
$\Delta I_L$	Nominal Peak – to – Peak Ripple of Inductor Current	4A
$\Delta V_o$	Nominal Peak – to – Peak Ripple of Output Voltage	1.2V
$L_m$	Magnetizing Inductance of the Transformer at Primary Side	10mH

## Section 1 - Steady – State Analysis and Concept Design

- a. The winding turns ratio can be expressed as:

$$1:n$$

The selected  $n$  value for this investigation is can be found through the following calculation:

$$\therefore \text{we assume: } D_{ON} < 50\%$$

$$n = \frac{V_o}{V_{in} D_{ON}} = \frac{12}{330 \times 0.5} = 0.0727$$

$$\therefore n > 0.0727 \text{ (is above steady – state)}$$

Hence, for this investigation the  $n$  value will be  $n = 0.085$ .

- b. The on-state duty ratio can be determined as follows:

$$D_{ON} = \frac{V_o}{nV_{in}} \rightarrow D_{ON} = \frac{12}{0.0727(330)} = 0.4278 = 42.78\% \text{ (2dp)}$$

$$\therefore D_{ON} \approx 0.4278 \dots = 42.78\%$$

- c. The computation for the on-state time can be determined as follows:

$$T_{ON} = \frac{D_{ON}}{f_{sw}} = \frac{0.4278}{(100 \times 10^3)} = 4.278 \times 10^{-6} \text{ s} = 4.278 \mu\text{s}$$

$$T_{sw} = \frac{T_{ON}}{D_{ON}} = \frac{(4.278 \times 10^{-6})}{0.4278} = 10 \times 10^{-6} \text{ s} = 10 \mu\text{s}$$

- d. The derivation for the inductance of the forward converter is:

$$T_{DOWN} = 5.722 \times 10^{-6}$$

$$L = \frac{V_o}{\Delta I_L} T_{DOWN} = \frac{12}{4} (4.278 \times 10^{-6}) = 12.83 \mu H$$

- e. The derivation for the capacitance is as follows:

$$C_o = \frac{\Delta I_L}{8 \Delta V_o f_{sw}} = \frac{4}{(8)(1.2)(100 \times 10^3)} = 4.166 \mu F$$

- f. The peak-to-peak ripple of  $i_{Lm}$  can be expressed as:

$$\Delta I_{in} = T_{ON} \frac{V_{in}}{L_m} = (4.278 \times 10^{-6}) \frac{330}{10 \times 10^{-3}} = 0.141174 A$$

$$\therefore i_{Lm} = \Delta I_{in} = 0.141 A$$

- g. The evaluation of the BCM condition regarding the levels of the output current and the load resistance were resolved as follows:

$$I_{o,crit} = \frac{\Delta I_L}{2} = \frac{4}{2} = 2 A$$

$$R_{crit} = \frac{V_o}{I_{o,crit}} = \frac{12}{2} = 6 \Omega$$

- h. The output voltage when the load resistance becomes  $6 \Omega$  with the duty ratio  $D_{ON}$  is applied (without loss consideration), is determined as follows;

Since, the circuit is operating in BCM, the voltage will not change. This can be illustrated using the formulation below:

$$(2T_{sw}L)V_o^2 + (-2V_{in}T_{sw}L)V_o + (-V_{in}^2RT_{ON}^2) = 0$$

$$(2 \times 10 \times 10^{-6} \times 20.1 \times 10^{-6})V_o^2 + (-2 \times 330 \times 10 \times 10^{-6} \times 20.1 \times 10^{-6})V_o + (-330^2 \times 6 \times (3.3 \times 10^{-6})^2) = 0$$

$$\therefore V_o = 11.952 V \approx 12 V$$

- i. The on-state duty ratio to maintain a specified output voltage of  $12 V$  without any loss consideration, with a load resistance becoming  $12 \Omega$  is:

$$(2T_{sw}L)V_o^2 + (-2V_{in}T_{sw}L)V_o + (-V_{in}^2RT_{ON}^2) = 0$$

$$\&$$

$$T_{ON} = D_{ON}T_{sw}$$

$$(2T_{sw}L)V_o^2 + (-2V_{in}T_{sw}L)V_o + (-V_{in}^2RT_{ON}^2) = 0$$

$$(2 \times 10 \times 10^{-6} \times 12^2 \times 20.1 \times 10^{-6}) + (-2 \times 330 \times 20.1 \times 10^{-6} \times 12 \times 10 \times 10^{-6}) - (330^2 \times 12 \times (3.3 \times 10^{-6})^2) = 0$$

$$D_{ON} = 0.2571 = 25.71\% (2dp)$$

## Section 2 - Simulation

- a. The following *figure 1*, displays the simulation model of the forward converter (buck and transformer arrangement):

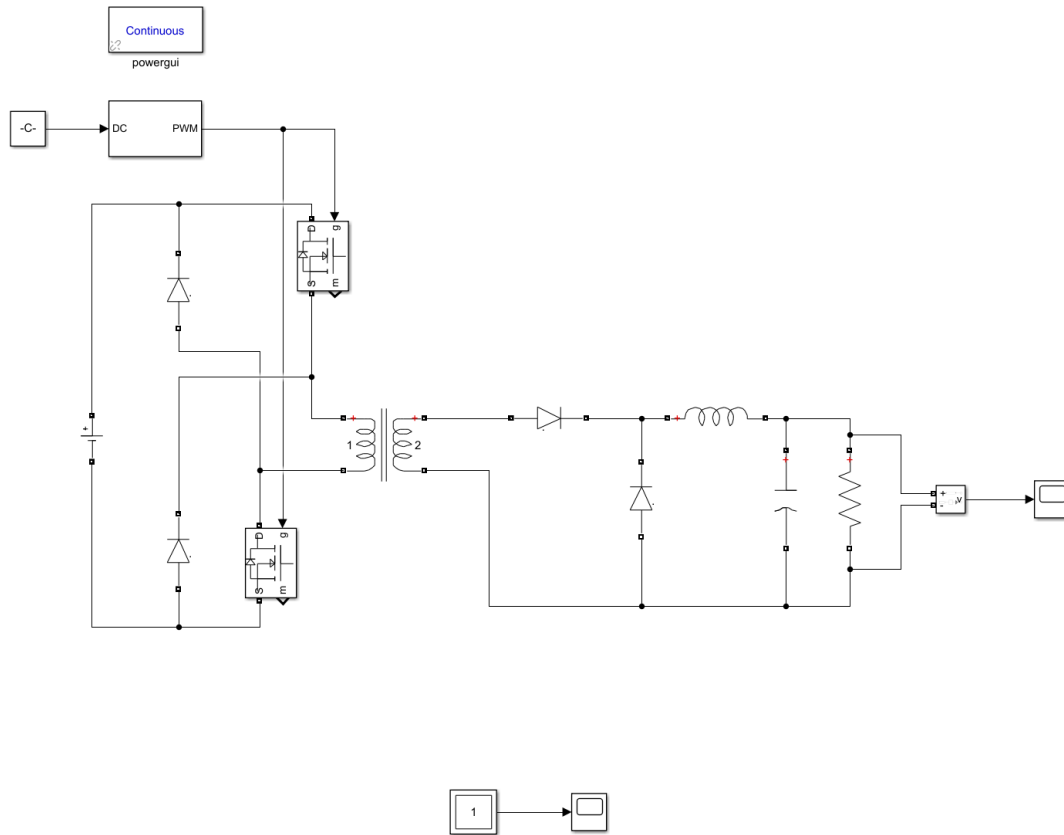


Figure 1: Forward Converter

b. The simulated results of  $v_{sw}$ ,  $i_L$  and  $v_o$  are illustrated as follows below respectively:

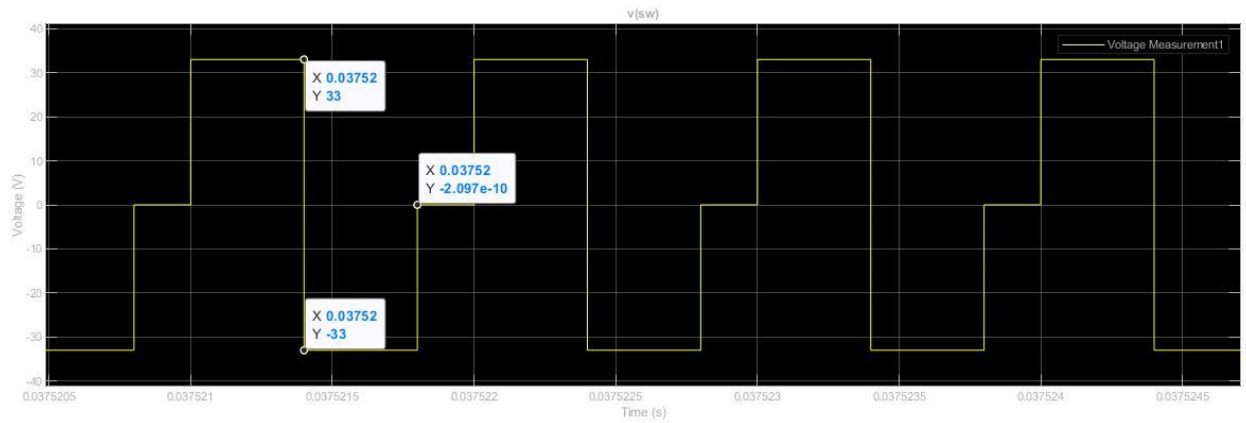


Figure 2: Voltage  $v_{sw}$

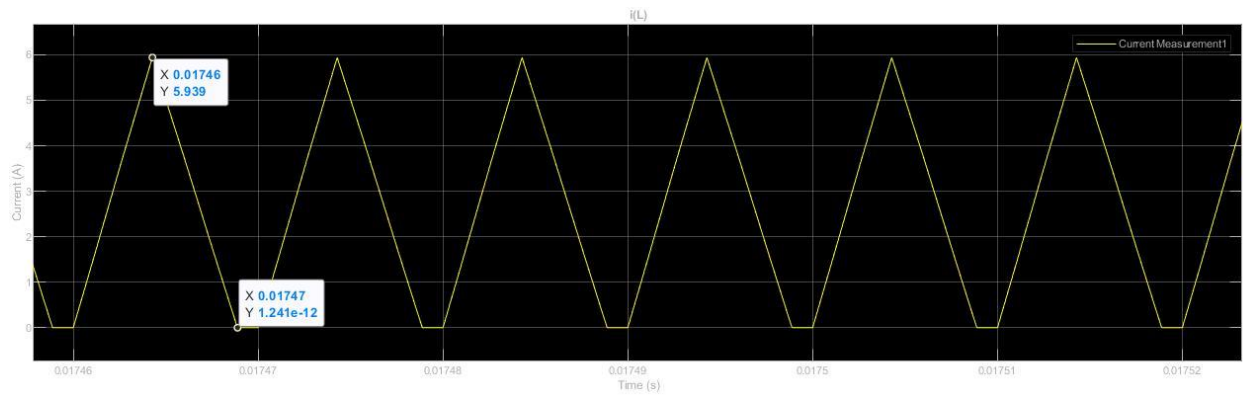


Figure 3: Current  $i_L$

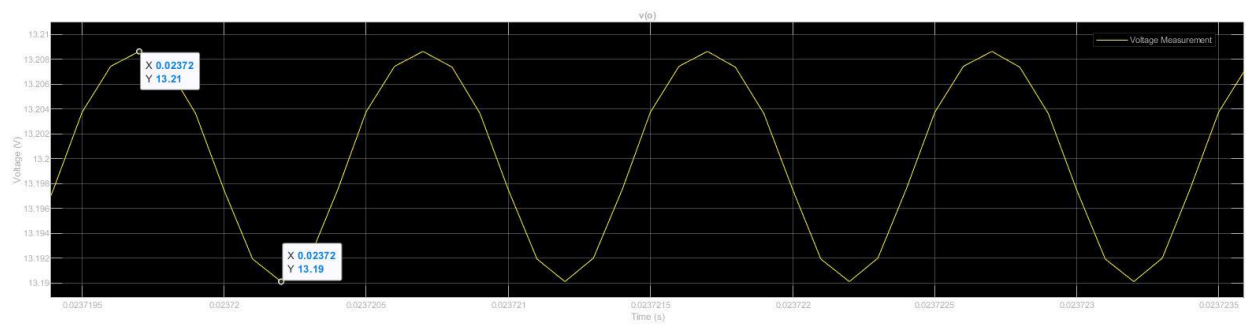


Figure 4: Voltage Output

c. The simulated results of  $v_{sw}$ ,  $i_{IN}$  and  $i_{Lm}$  are illustrated as follows below respectively:

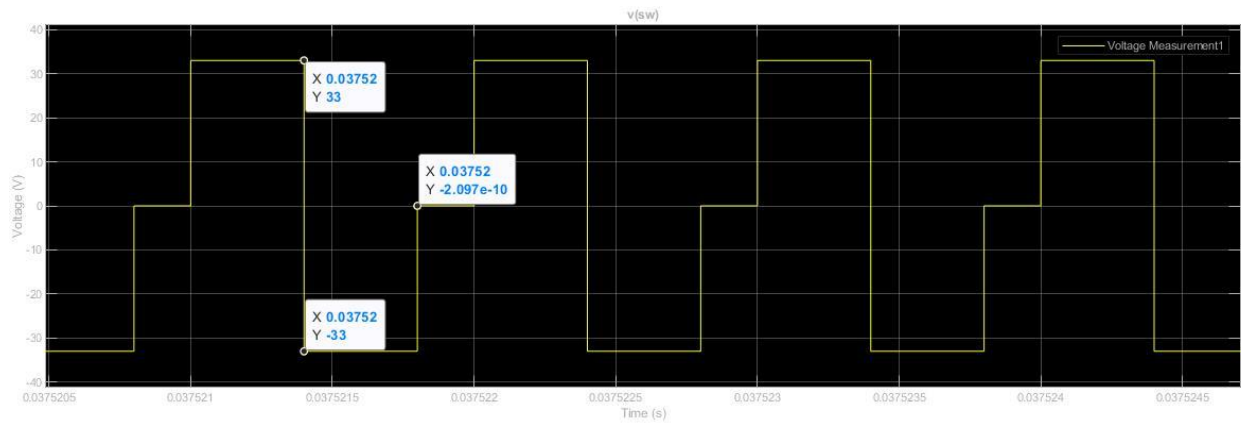


Figure 5: Voltage  $v_{sw}$

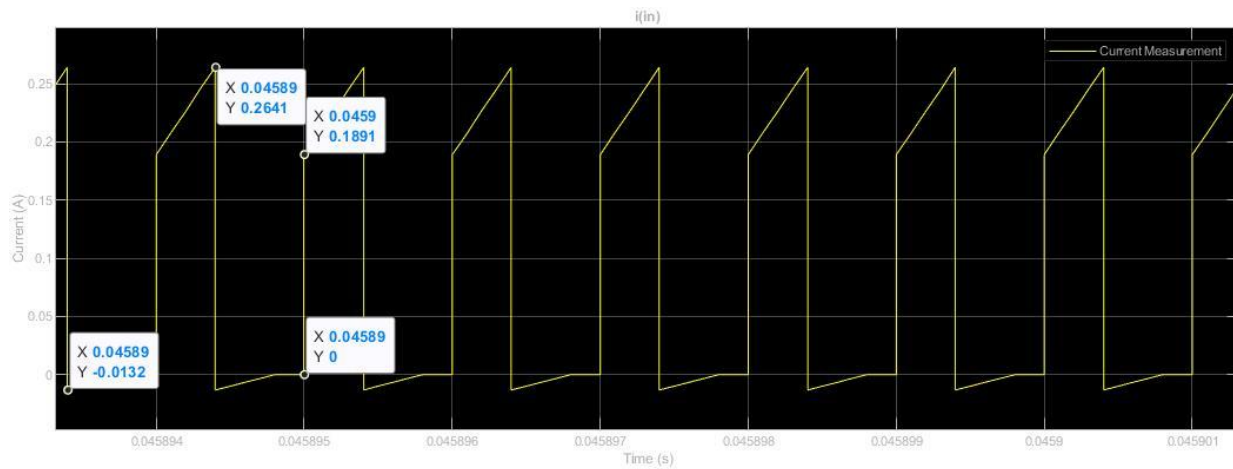


Figure 6: Current Input

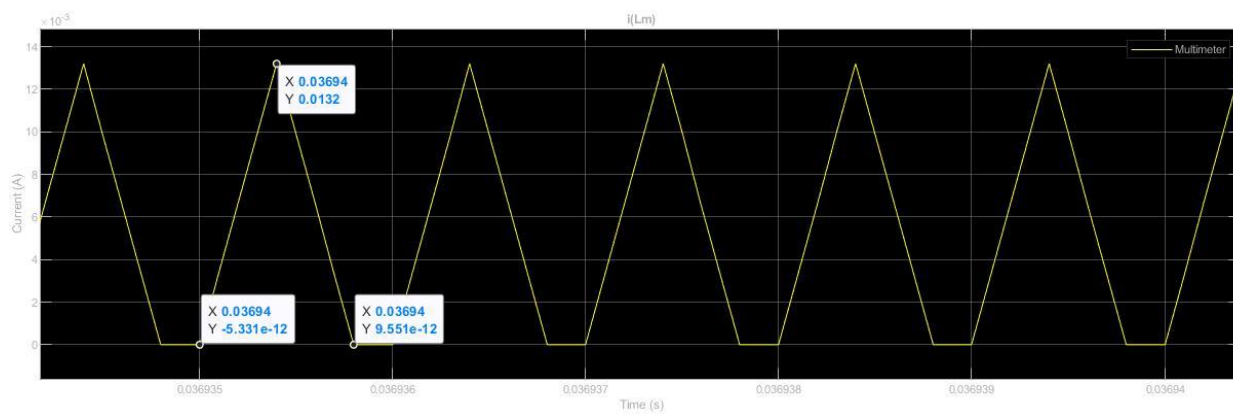


Figure 7: Current  $i_{Lm}$

- d. Simulation confirms the design of the nominal condition partially. The voltage output is overshooting the expected 12V due to the selected  $n$  value along with the  $D_{ON}$  and the diode configuration. See *figure 8* for the diode options selected for the simulation design.

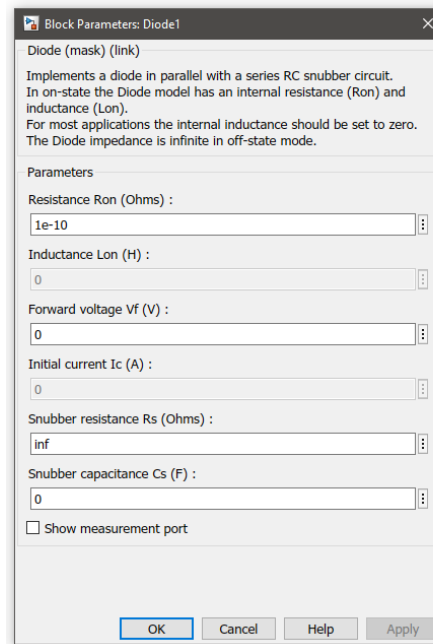


Figure 8: Diode Configuration

The voltage output trace can be smoother by increasing the PWM sample time and period. The configuration for the PMW is specified in *figure 9* below.

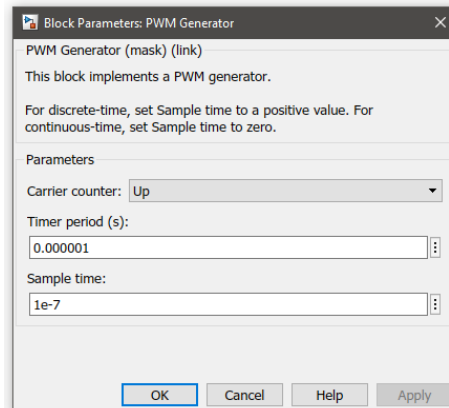


Figure 9: PWM Configuration

The values of  $i_{Lm}$  current may also be altered with the above selection explaining the discrepancy from the expected peak value of 0.141A approximately.



The voltage  $v_{sw}$  is as expected from the trace with specifications from the transformer causing negligible discrepancies. The transformer specifications is illustrated in *figure 10*.

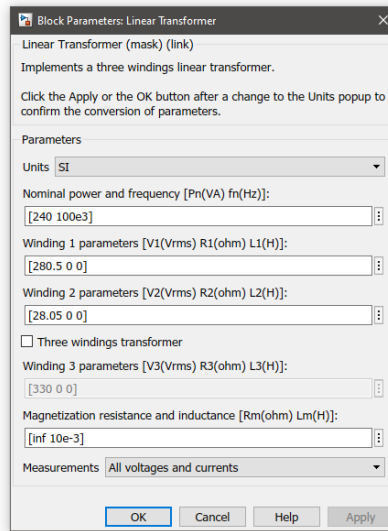


Figure 10: Transformer Specifications

The current input is also as the investigation expected from the parameters calculated and the shape of the trace that was outputted from the scope.

- e. The simulation of the results that was investigated in *Section 1 Part h* of the investigation are as follows:

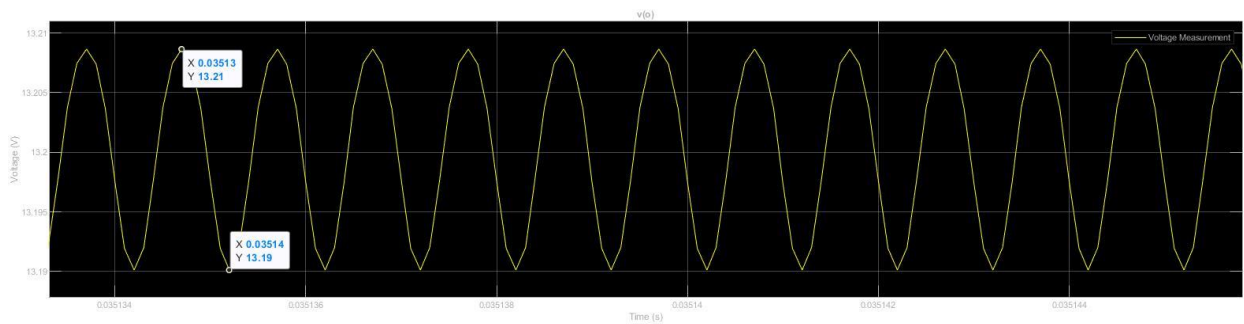


Figure 11: Voltage Output – 6 ohms

As expected, the voltage illustrates the same voltage in *Part a* of this section, *Section 2*. This is due to the operation of the circuit in BCM.

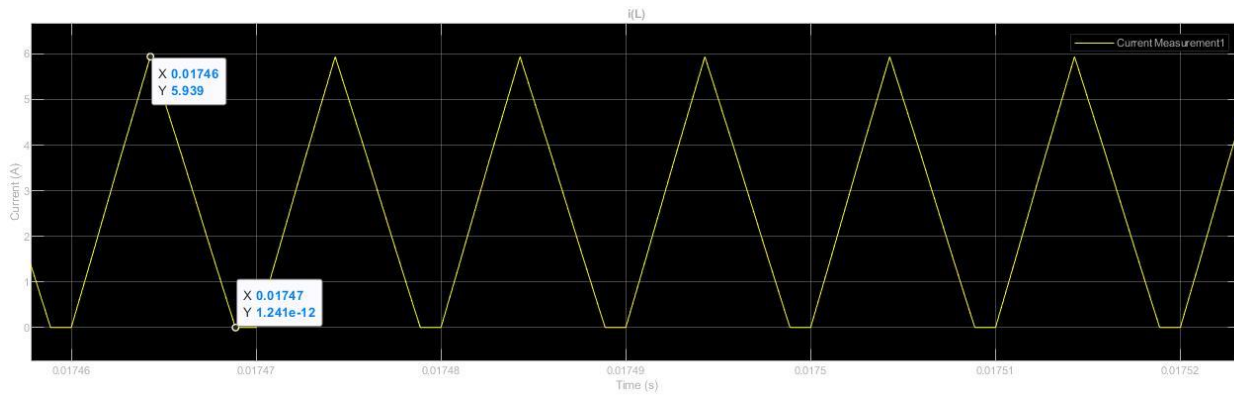


Figure 12: Current Output - 6 ohms

As expected,  $i_L$  overshoots slightly from the expected 4A peak-to-peak with the explanation from the previous question. Furthermore, the fluctuation with a resistance of six ohms moves between values zero to approximately six.

- f. The condition described in *Section 1, Part i* was simulated and the following highlights the results:

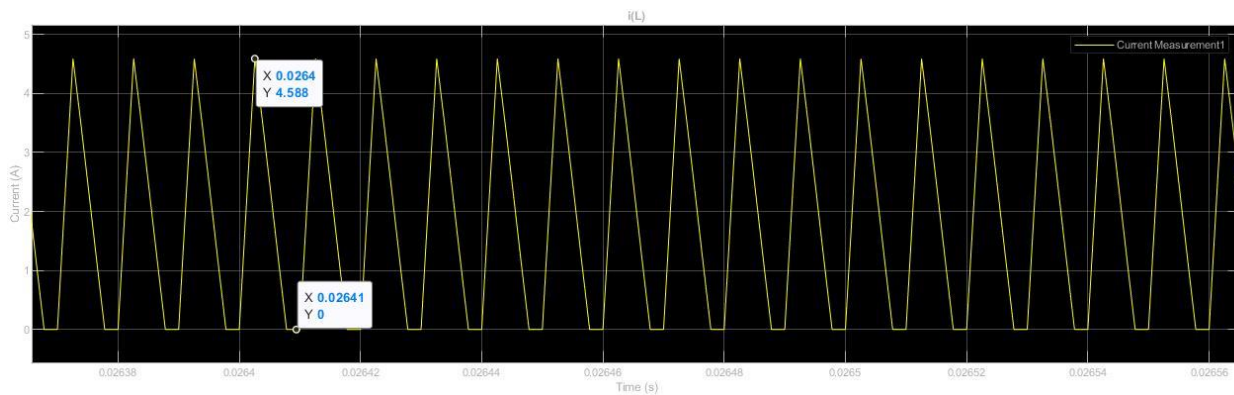


Figure 13: Current  $i_L$

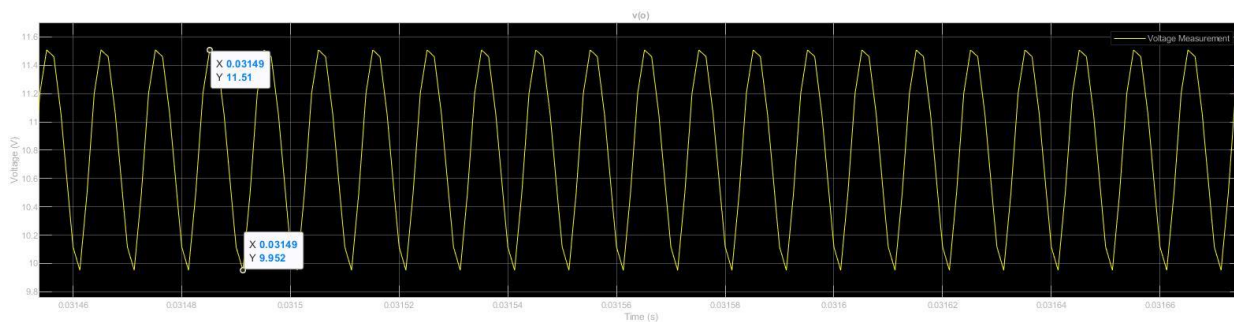


Figure 14: Voltage Output

## Bibliography

Hart, D. W. (2010). *Power Electronics*. Valparaiso, Indiana: Pearson Education, Inc.